
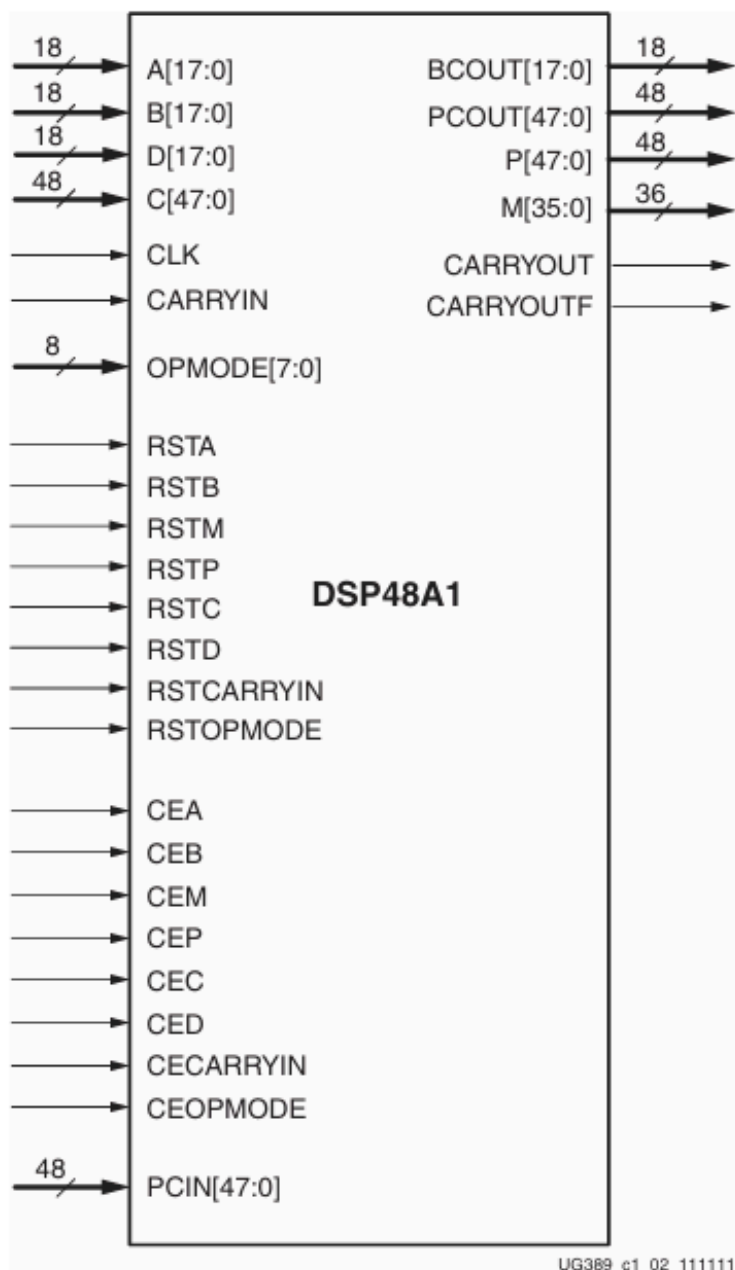


Spartan6 - DSP48A1

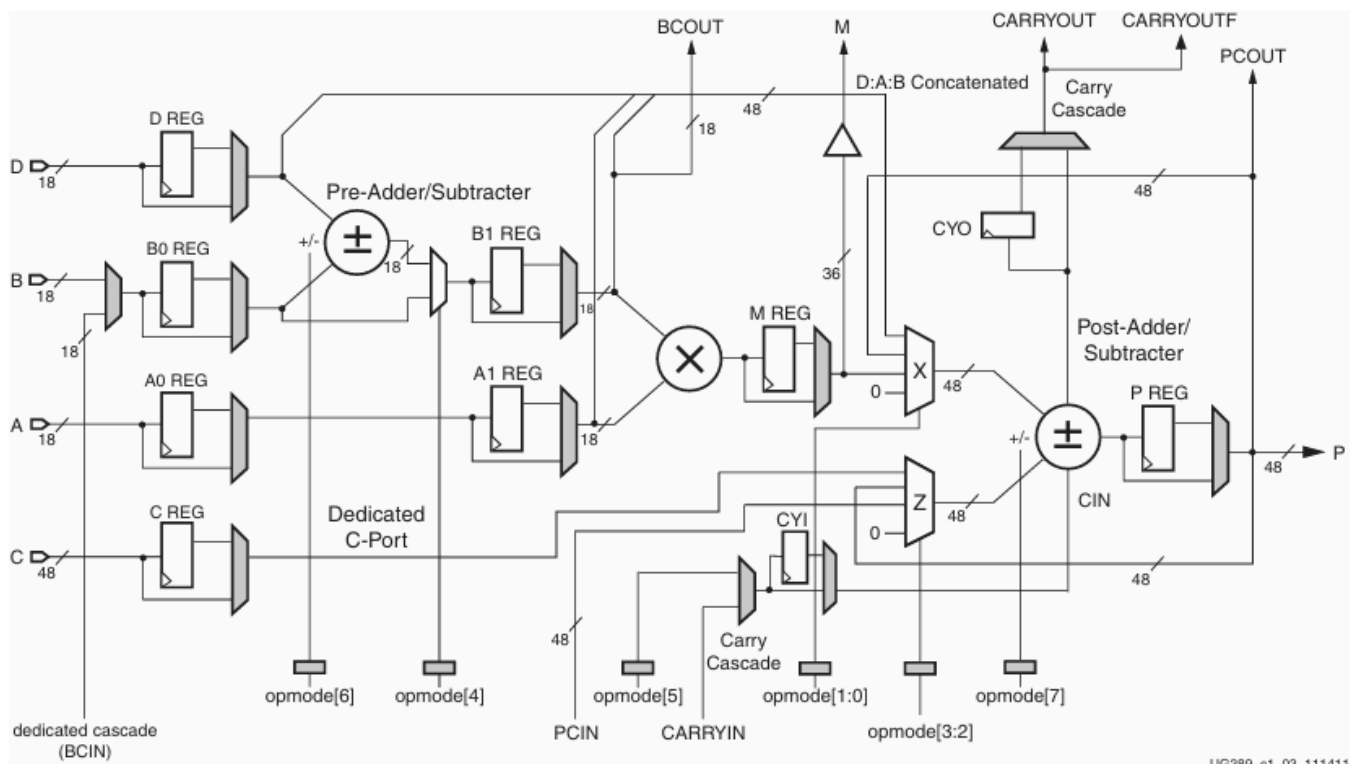

UG389_c1_02_111111



UG389_c1_03_111411

RTL CODE

DSP48A1

```
module DSP48A1 #(
    parameter AOREG = 0,
    parameter A1REG = 1,
    parameter BOREG = 0,
    parameter B1REG = 1,
    parameter CREG = 1,
    parameter DREG = 1,
    parameter MREG = 1,
    parameter PREG = 1,
    parameter CARRYINREG = 1,
    parameter CARRYOUTREG = 1,
    parameter OPMODEREG = 1,
    parameter CARRYINSEL = "OPMODE5",
    parameter B_INPUT = "DIRECT" ,
    parameter RSTTYPE = "SYNC"
)(
    input [17:0] A,
    input [17:0] B,
    input [47:0] C,
    input [17:0] D,
    input      CARRYIN,
    output [35:0] M,
    output [47:0] P,
    output      CARRYOUT,
    output      CARRYOUTF,
    input      CLK,
    input [7:0] OPMODE,
    input      CEA,
    input      CEB,
    input      CEC,
    input      CECARRYIN,
    input      CED,
    input      CEM,
    input      CEOPMODE,
    input      CEP,
    input      RSTA, input      RSTB,
    input      RSTC,
    input      RSTCARRYIN,
    input      RSTD,
    input      RSTM,
    input      RSTOPMODE,
    input      RSTP,
    input [17:0] BCIN,
    input [47:0] PCIN,
    output [17:0] BCOUT,
    output [47:0] PCOUT
);
```

RTL CODE

INTERNAL WIRES

```
wire [17:0] A0_out, A1_out, A0_reg_out, A1_reg_out;
wire [17:0] B0_out, B1_out, B_mux_out, B0_reg_out, B1_reg_out;
wire [47:0] C_out, C_reg_out;
wire [17:0] D_out, D_reg_out;
wire [7:0] OPMODE_out, OPMODE_reg_out;
wire CARRYIN_out, CARRYIN_reg_out, CARRYIN_mux_out;
wire CARRYOUT_out, CARRYOUT_reg_out;
wire [35:0] M_out, M_reg_out, Multiplier_out;
wire [17:0] pre_adder_out, OPMODE4_MUX_out;
wire [47:0] post_adder_out, Z_mux_out, X_mux_out, P_reg_out,
Concatenate_wires;
```

A PATH

```
REG #(.WIDTH(18), .RSTTYPE(RSTTYPE)) A0_reg (
    .clk(CLK), .CE(CEA), .rst(RSTA), .data_in(A), .data_out(A0_reg_out)
);
MUX #(.WIDTH(18), .NUM_INPUTS(2)) A0_mux (
    .IN0(A), .IN1(A0_reg_out), .IN2(18'b0), .IN3(18'b0), .sel(A0REG), .data_out(A0_out)
);
REG #(.WIDTH(18), .RSTTYPE(RSTTYPE)) A1_reg (
    .clk(CLK), .CE(CEA), .rst(RSTA), .data_in(A0_out), .data_out(A1_reg_out)
);
MUX #(.WIDTH(18), .NUM_INPUTS(2)) A1_mux (
    .IN0(A0_out), .IN1(A1_reg_out), .IN2(18'b0), .IN3(18'b0), .sel(A1REG), .data_out(A1_out)
);
```

B PATH

```
MUX #(.WIDTH(18), .NUM_INPUTS(2)) B_mux (
    .IN0(B), .IN1(BCIN), .IN2(18'b0), .IN3(18'b0), .sel(B_INPUT == "CASCADE"), .data_out(B_mux_out)
);
REG #(.WIDTH(18), .RSTTYPE(RSTTYPE)) B0_reg (
    .clk(CLK), .CE(CEB), .rst(RSTB), .data_in(B_mux_out), .data_out(B0_reg_out)
);
MUX #(.WIDTH(18), .NUM_INPUTS(2)) B0_mux (
    .IN0(B_mux_out), .IN1(B0_reg_out), .IN2(18'b0), .IN3(18'b0), .sel(B0REG), .data_out(B0_out)
);
REG #(.WIDTH(18), .RSTTYPE(RSTTYPE)) B1_reg (
    .clk(CLK), .CE(CEB), .rst(RSTB), .data_in(OPMODE4_MUX_out), .data_out(B1_reg_out)
);
MUX #(.WIDTH(18), .NUM_INPUTS(2)) B1_mux (
    .IN0(OPMODE4_MUX_out), .IN1(B1_reg_out), .IN2(18'b0), .IN3(18'b0), .sel(B1REG), .data_out(B1_out)
);
assign BCOUT = B1_out;
```

RTL CODE

C PATH

```
REG #(.WIDTH(48), .RSTTYPE(RSTTYPE)) C_reg (  
    .clk(CLK), .CE(CEC), .rst(RSTC), .data_in(C), .data_out(C_reg_out)  
);  
MUX #(.WIDTH(48), .NUM_INPUTS(2)) C_mux (  
    .IN0(C), .IN1(C_reg_out), .IN2(48'b0), .IN3(48'b0), .sel(CREG),  
.data_out(C_out)  
);
```

D PATH

```
REG #(.WIDTH(18), .RSTTYPE(RSTTYPE)) D_reg (  
    .clk(CLK), .CE(CED), .rst(RSTD), .data_in(D), .data_out(D_reg_out)  
);  
MUX #(.WIDTH(18), .NUM_INPUTS(2)) D_mux (  
    .IN0(D), .IN1(D_reg_out), .IN2(18'b0), .IN3(18'b0), .sel(DREG), .data_out(D_out)  
);
```

OPMODE

```
REG #(.WIDTH(8), .RSTTYPE(RSTTYPE)) OPMODE_reg (  
    .clk(CLK), .CE(CEOPMODE), .rst(RSTOPMODE), .data_in(OPMODE), .data_out(OPMODE_reg_out)  
);  
MUX #(.WIDTH(8), .NUM_INPUTS(2)) OPMODE_mux (  
    .IN0(OPMODE), .IN1(OPMODE_reg_out), .IN2(8'b0), .IN3(8'b0), .sel(OPMODEREG), .data_out(OPMODE_out)  
);
```

CARRY-IN

```
MUX #(.WIDTH(1), .NUM_INPUTS(2)) CARRYIN_mux (  
    .IN0(CARRYIN), .IN1(OPMODE_out[5]), .IN2(1'b0), .IN3(1'b0), .sel(CARRYINSEL == "OPMODE5"),  
.data_out(CARRYIN_mux_out)  
);  
REG #(.WIDTH(1), .RSTTYPE(RSTTYPE)) CARRYIN_reg (  
    .clk(CLK), .CE(CECARRYIN), .rst(RSTCARRYIN), .data_in(CARRYIN_mux_out),  
.data_out(CARRYIN_reg_out)  
);  
MUX #(.WIDTH(1), .NUM_INPUTS(2)) CARRYIN_final_mux (  
    .IN0(CARRYIN_mux_out), .IN1(CARRYIN_reg_out), .IN2(1'b0), .IN3(1'b0), .sel(CARRYINREG),  
.data_out(CARRYIN_out)  
);
```

PRE-ADDER/SUBTRACTOR

```
assign pre_adder_out = (OPMODE_out[6]) ? (D_out - B0_out) : (D_out + B0_out);
```

OPMODE4 MUX

```
assign OPMODE4_MUX_out = (OPMODE_out[4]) ? pre_adder_out : B0_out;
```

RTL CODE

MULTIPLIER

```
assign Multiplier_out = A1_out * B1_out;
    REG #(.WIDTH(36), .RSTTYPE(RSTTYPE)) M_reg (
        .clk(CLK), .CE(CEM), .rst(RSTM), .data_in(Multiplier_out), .data_out(M_reg_out)
    );
    MUX #(.WIDTH(36), .NUM_INPUTS(2)) M_mux (
        .IN0(Multiplier_out), .IN1(M_reg_out), .IN2(36'b0), .IN3(36'b0), .sel(MREG),
        .data_out(M_out)
    );
    assign M = M_out;
```

CONCATENATE WIRES

```
assign Concatenate_wires = {D_out[11:0], A1_out, B1_out};
```

X MUX

```
MUX #(.WIDTH(48), .NUM_INPUTS(4)) X_mux (
    .IN0(48'b0),
    .IN1({12'b0, M_out}),
    .IN2(P),
    .IN3(Concatenate_wires),
    .sel(OPMODE_out[1:0]), .data_out(X_mux_out)
);
```

Z MUX

```
MUX #(.WIDTH(48), .NUM_INPUTS(4)) Z_mux (
    .IN0(48'b0),
    .IN1(PCIN),
    .IN2(P),
    .IN3(C_out),
    .sel(OPMODE_out[3:2]), .data_out(Z_mux_out)
);
```

POST-ADDER/SUBTRACTOR

```
assign {CARRYOUT_out, post_adder_out} = (OPMODE_out[7]) ?
    (Z_mux_out - (X_mux_out + CARRYIN_out)) :
    (Z_mux_out + X_mux_out + CARRYIN_out);
```

CARRYOUT

```
REG #(.WIDTH(1), .RSTTYPE(RSTTYPE)) CARRYOUT_reg (
    .clk(CLK), .CE(CECARRYIN), .rst(RSTCARRYIN), .data_in(CARRYOUT_out), .data_out(CARRYOUT_reg_out)
);
MUX #(.WIDTH(1), .NUM_INPUTS(2)) CARRYOUT_mux (
    .IN0(CARRYOUT_out), .IN1(CARRYOUT_reg_out), .IN2(1'b0), .IN3(1'b0), .sel(CARRYOUTREG), .data_out(CARRYOUT)
);
assign CARRYOUTF = CARRYOUT;
```

RTL CODE

P OUTPUT

```
REG #(.WIDTH(48), .RSTTYPE(RSTTYPE)) P_reg (  
    .clk(CLK), .CE(CEP), .rst(RSTP), .data_in(post_adder_out), .data_out(P_reg_out)  
);  
MUX #(.WIDTH(48), .NUM_INPUTS(2)) P_mux (  
    .IN0(post_adder_out), .IN1(P_reg_out), .IN2(48'b0), .IN3(48'b0), .sel(PREG),  
.data_out(P)  
);  
assign PCOUT = P;
```

MODULES

MUX

```
module MUX #(  
    parameter WIDTH = 1, // Width of the Mux,  
    parameter NUM_INPUTS = 2 // Default Number of Inputs  
)(  
    input [WIDTH-1:0] IN0,  
    input [WIDTH-1:0] IN1,  
    input [WIDTH-1:0] IN2,  
    input [WIDTH-1:0] IN3,  
    input [$clog2(NUM_INPUTS)-1:0] sel,  
    output reg [WIDTH-1:0] data_out  
);  
always @(*) begin  
    case (sel)  
        2'b00: data_out = IN0;  
        2'b01: data_out = IN1;  
        2'b10: data_out = IN2;  
        2'b11: data_out = IN3;  
        default: data_out = {WIDTH{1'b0}}; // Default case  
    endcase  
end  
  
endmodule
```

REG

```
module REG #(
    parameter WIDTH = 1, // Width of the register,
    parameter RSSTYPE = "SYNC" // Default TYPE of reset
)(
    input wire clk,CE,
    input wire rst,
    input wire [WIDTH-1:0] data_in,
    output reg [WIDTH-1:0] data_out
);
generate
    if (RSSTYPE == "ASYNC") begin
        always @(posedge clk or posedge rst) begin
            if (rst)
                data_out <= {WIDTH{1'b0}};
            else if (CE)
                data_out <= data_in;
        end
    end
    else begin // If -> RSSTYPE = "SYNC"
        always @(posedge clk) begin
            if (rst)
                data_out <= {WIDTH{1'b0}};
            else if (CE)
                data_out <= data_in;
        end
    end
endgenerate

endmodule
```

TESTBENCH CODE

PARAMETERS

```
parameter AOREG = 0;
parameter A1REG = 1;
parameter BOREG = 0;
parameter B1REG = 1;
parameter CREG = 1;
parameter DREG = 1;
parameter MREG = 1;
parameter PREG = 1;
parameter CARRYINREG = 1;
parameter CARRYOUTREG = 1;
parameter OPMODEREG = 1;
parameter CARRYINSEL = "OPMODE5";
parameter B_INPUT = "DIRECT";
parameter RSSTYPE = "SYNC";
```


DATA PORTS

```
reg [17:0] A;
reg [17:0] B;
reg [47:0] C;
reg [17:0] D;
reg      CARRYIN;

wire [35:0] M;
wire [47:0] P;
wire      CARRYOUT;
wire      CARRYOUTF;

reg      CLK;
reg [7:0] OPMODE;
reg      CEA;
reg      CEB;
reg      CEC;
reg      CECARRYIN;
reg      CED;
reg      CEM;
reg      CEOPMODE;
reg      CEP;

reg      RSTA;
reg      RSTB;
reg      RSTC;
reg      RSTCARRYIN;
reg      RSTD;
reg      RSTM;
reg      RSTOPMODE;
reg      RSTP;

reg [17:0] BCIN;
reg [47:0] PCIN;
wire [17:0] BCOUT;
wire [47:0] PCOUT;
```

CLOCK GENERATION

```
initial begin
    CLK = 0;
    forever #1 CLK = ~CLK; // 2 time units clock period
end
```

INSTANTIATE THE DSP48A1 MODULE

```
DSP48A1 #(
    .A0REG(A0REG),
    .A1REG(A1REG),
    .B0REG(B0REG),
    .B1REG(B1REG),
    .CREG(CREG),
    .DREG(DREG),
    .MREG(MREG),
    .PREG(PREG),
    .CARRYINREG(CARRYINREG),
    .CARRYOUTREG(CARRYOUTREG),
    .OPMODEREG(OPMODEREG),
    .CARRYINSEL(CARRYINSEL),
    .B_INPUT(B_INPUT),
    .RSTTYPE(RSTTYPE)
) uut (
    .A(A),
    .B(B),
    .C(C),
    .D(D),
    .CARRYIN(CARRYIN),
    .M(M),
    .P(P),
    .CARRYOUT(CARRYOUT),
    .CARRYOUTF(CARRYOUTF),
    .CLK(CLK),
    .OPMODE(OPMODE),
    .CEA(CEA),
    .CEB(CEB),
    .CEC(CEC),
    .CECARRYIN(CECARRYIN),
    .CED(CED),
    .CEM(CEM),
    .CEOPMODE(CEOPMODE),
    .CEP(CEP),
    .RSTA(RSTA),
    .RSTB(RSTB),
    .RSTC(RSTC),
    .RSTCARRYIN(RSTCARRYIN),
    .RSTD(RSTD),
    .RSTM(RSTM),
    .RSTOPMODE(RSTOPMODE),
    .RSTP(RSTP),
    .BCIN(BCIN),
    .PCIN(PCIN),
    .BCOUT(BCOUT),
    .PCOUT(PCOUT)
);
```

STIMULUS GENERATION (INITIAL BLOCK)

```
initial begin
    // Initialize all inputs
    A = 0; B = 0; C = 0; D = 0; CARRYIN = 0; OPMODE = 0; BCIN = 0; PCIN = 0;
    CLK = 0; CEA = 0; CEB = 0; CEC = 0; CECARRYIN = 0; CED = 0; CEM = 0; CEOPMODE = 0; CEP = 0;
    //Verify Reset Operation
    RSTA = 1; RSTB = 1; RSTC = 1; RSTCARRYIN = 1; RSTD = 1; RSTM = 1; RSTOPMODE = 1; RSTP = 1;

    A = $random; B = $random; C = $random; D = $random; CARRYIN = $random;
    OPMODE = $random;
    CEA = $random; CEB = $random; CEC = $random;
    CECARRYIN = $random; CED = $random; CEM = $random; CEOPMODE = $random; CEP = $random;
    @ (negedge CLK);
    if (M == 0 && P == 0 && CARRYOUT == 0 && CARRYOUTF == 0 && BCOUT == 0 && PCOUT == 0) begin
        $display("Reset successful, outputs are zero.");
    end else begin
        $display("Reset failed, outputs are not zero.\n M: %h, P: %h, CARRYOUT: %b, CARRYOUTF: %b,
BCOUT: %h, PCOUT: %h", M, P, CARRYOUT, CARRYOUTF, BCOUT, PCOUT);
        $stop;
    end

    // Deassert reset
    RSTA = 0; RSTB = 0; RSTC = 0; RSTCARRYIN = 0; RSTD = 0; RSTM = 0; RSTOPMODE = 0; RSTP = 0;
    CEA = 1; CEB = 1; CEC = 1; CECARRYIN = 1; CED = 1; CEM = 1; CEOPMODE = 1; CEP = 1;
```

VERIFY DSP PATH 1

```
OPMODE = 8'b11011101;
A = 20; B = 10; C = 350; D = 25;
BCIN= $random; PCIN = $random; CARRYIN = $random;
repeat(4) @(negedge CLK);
if (BCOUT == 18'hf && M == 36'h12c && P == 48'h32 && PCOUT == 48'h32 && CARRYOUT == 0 &&
CARRYOUTF == 0) begin
    $display("DSP Path 1 successful");
end else begin
    $display("DSP Path 1 failed");
    $stop;
end
```

VERIFY DSP PATH 2

```
OPMODE = 8'b00010000;
A = 20; B = 10; C = 350; D = 25;
BCIN= $random; PCIN = $random; CARRYIN = $random;
repeat(3) @(negedge CLK);
if (BCOUT == 18'h23 && M == 36'h2bc && P == 0 && PCOUT == 0 && CARRYOUT == 0 && CARRYOUTF ==
0) begin
    $display("DSP Path 2 successful");
end else begin
    $display("DSP Path 2 failed");
    $stop;
end
```

VERIFY DSP PATH 3


```
OPMODE = 8'b00001010;
A = 20; B = 10; C = 350; D = 25;
BCIN= $random; PCIN = $random; CARRYIN = $random;
repeat(3) @(negedge CLK);
if (BCOUT == 18'ha && M == 36'hc8 && P == P && PCOUT == P && CARRYOUT == CARRYOUT &&
CARRYOUTF == CARRYOUTF) begin
    $display("DSP Path 3 successful");
end else begin
    $display("DSP Path 3 failed");
    $stop;
end
end
```

VERIFY DSP PATH 4


```
OPMODE = 8'b10100111;
A = 5; B = 6; C = 350; D = 25; PCIN = 3000;
BCIN= $random; CARRYIN = $random;
repeat(3) @(negedge CLK);
if (BCOUT == 18'h6 && M == 36'h1e && P == 48'hfe6fffec0bb1 && PCOUT == 48'hfe6fffec0bb1 &&
CARRYOUT == 1 && CARRYOUTF == 1) begin
    $display("DSP Path 4 successful");
end else begin
    $display("DSP Path 4 failed");
    $stop;
end
end
```

SIMULATION RESULTS


VERIFY RESET

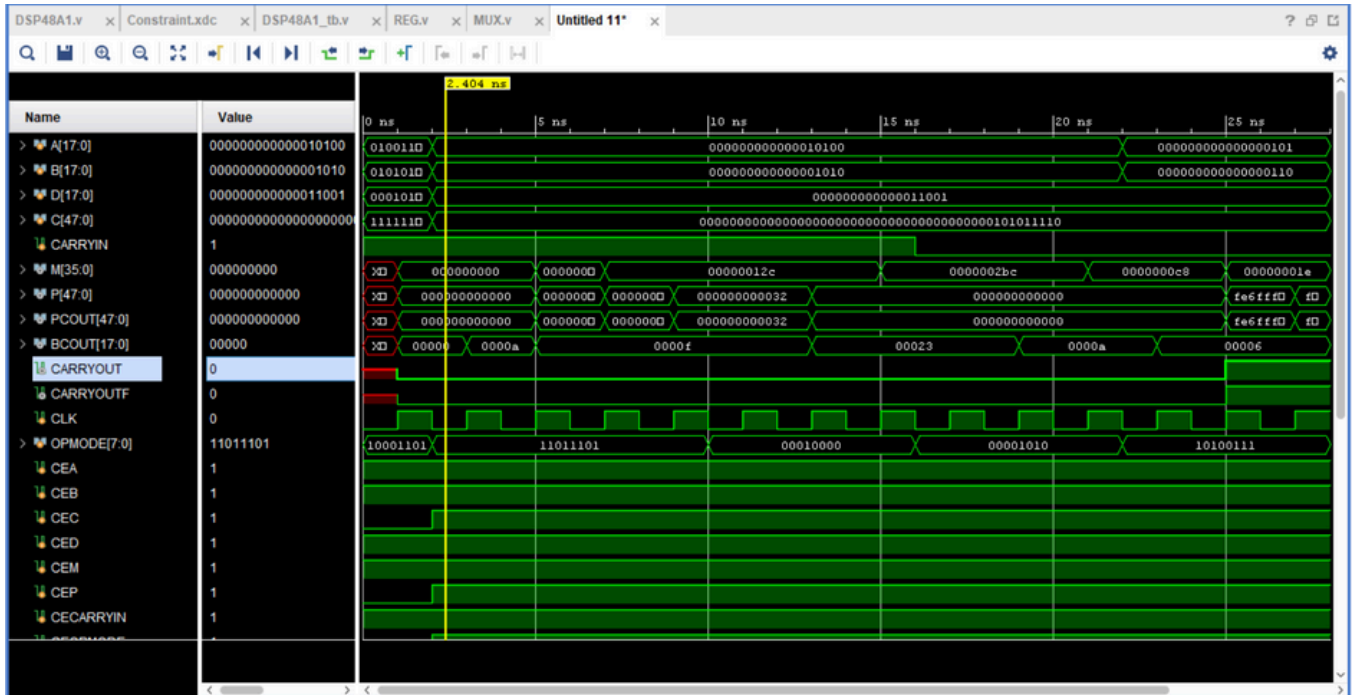


VERIFY DSP PATH 1

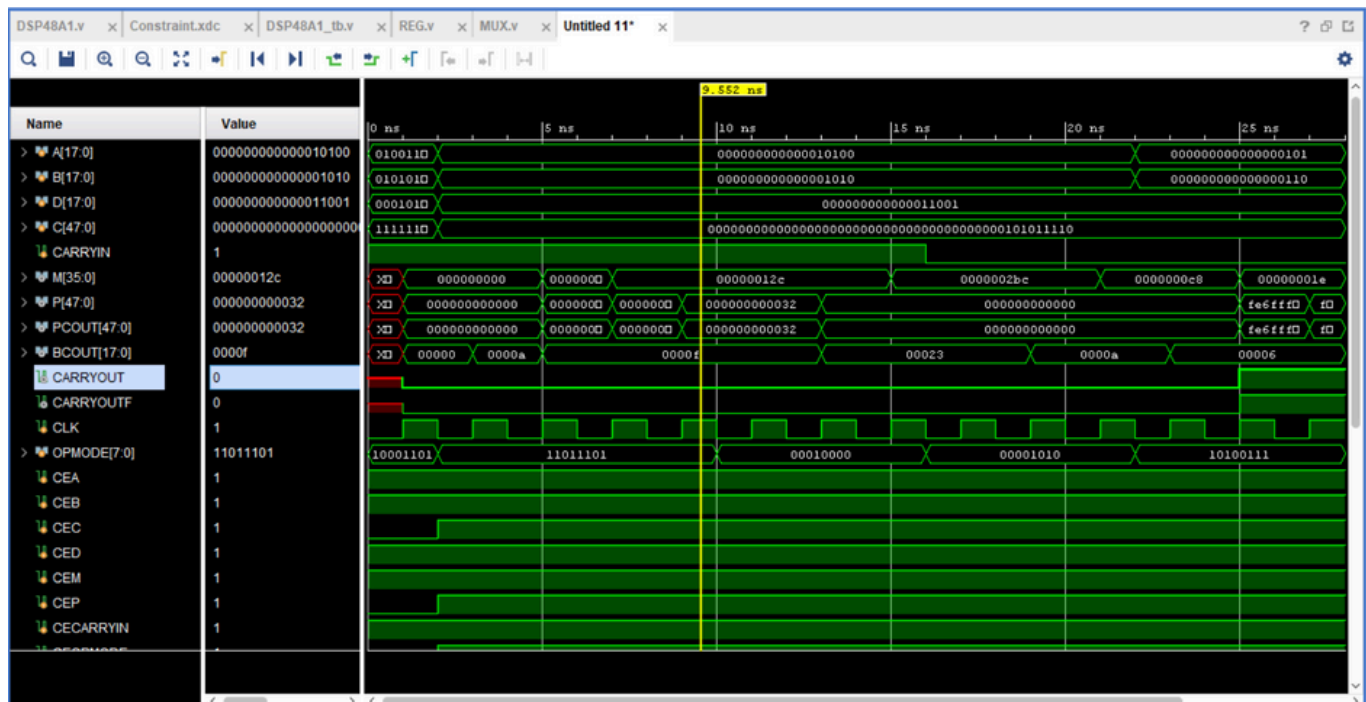


VERIFY DSP PATH 2

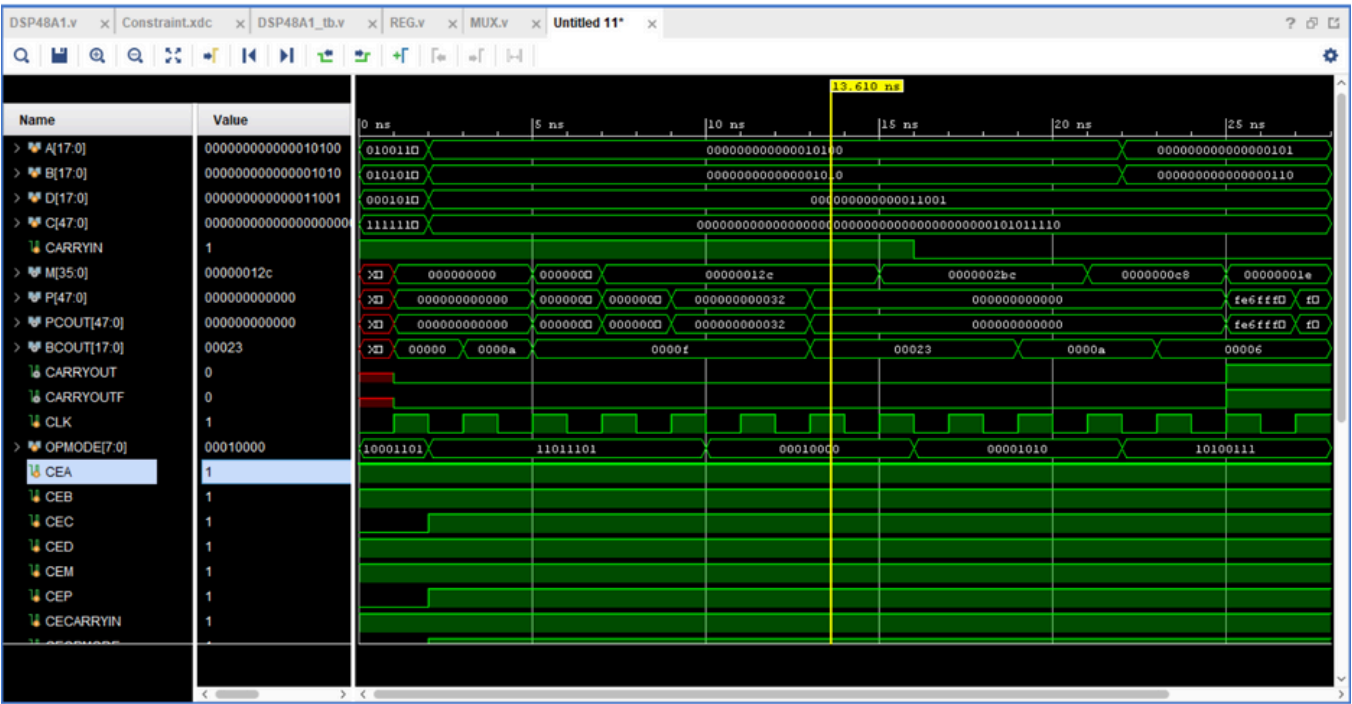


VERIFY DSP PATH 3

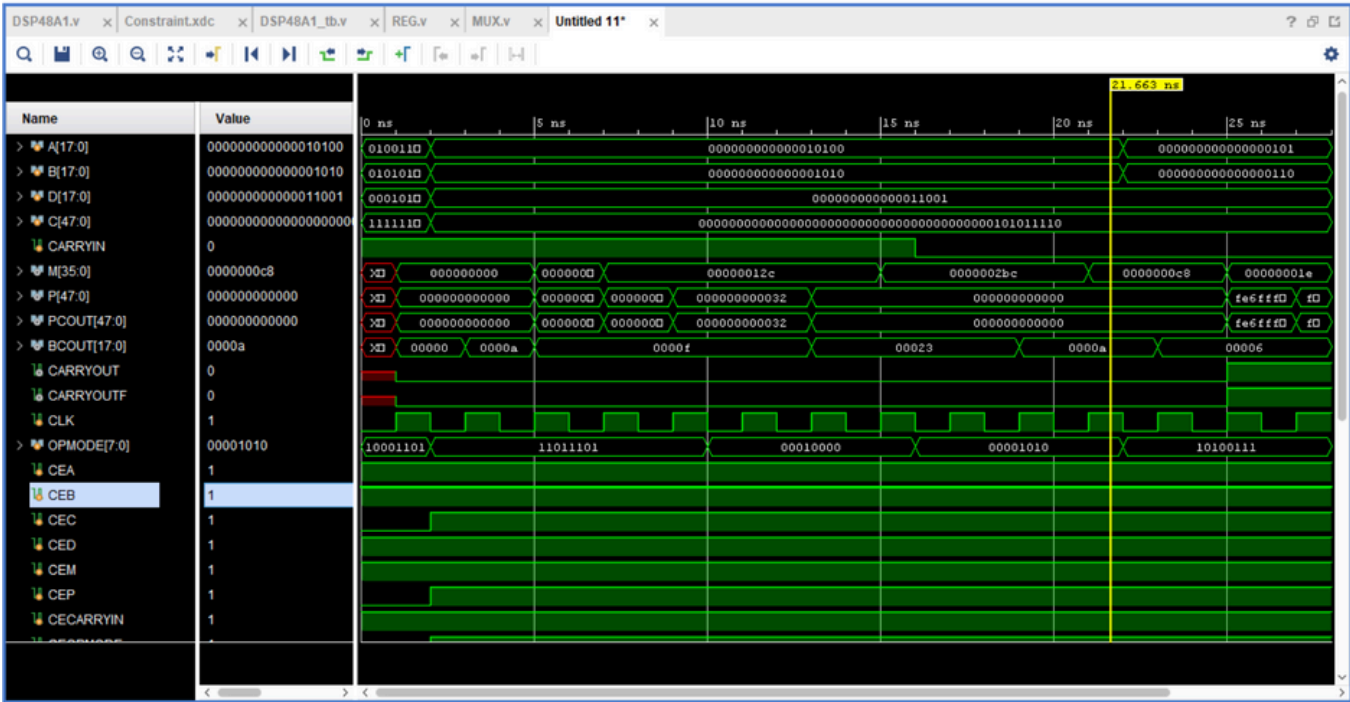

VERIFY DSP PATH 4

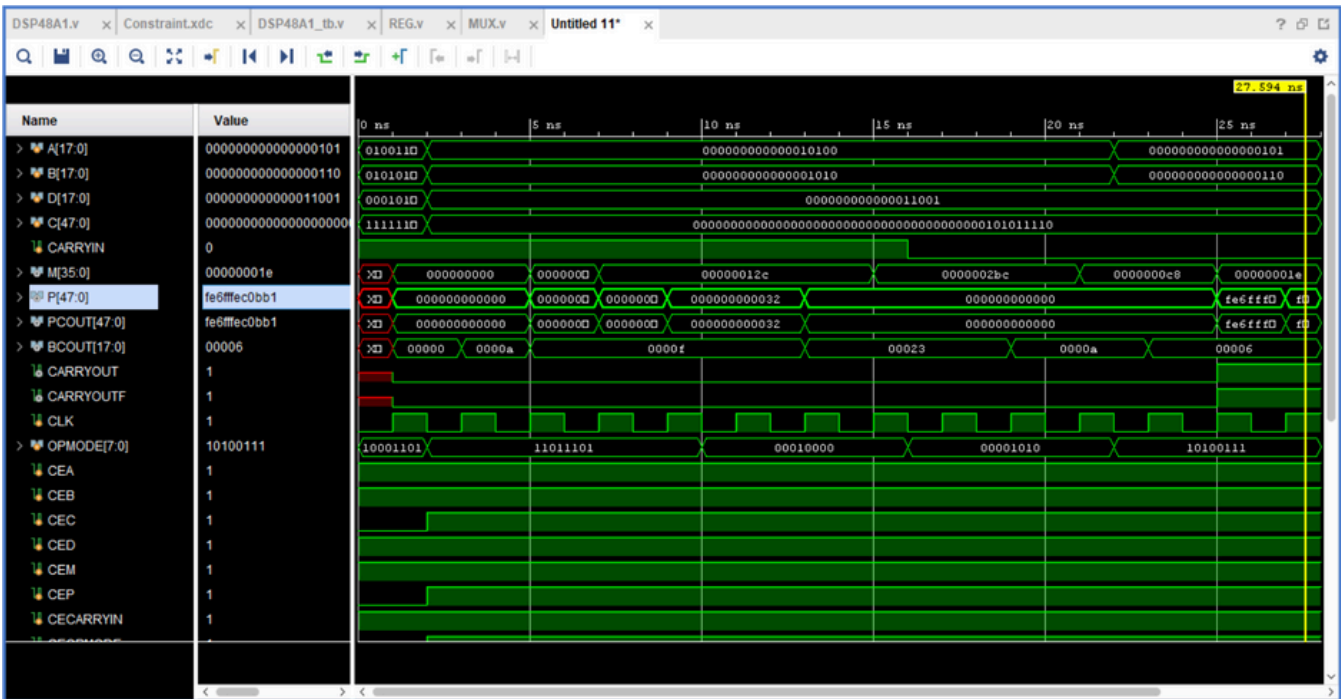


ELABORATION SCHEMATIC

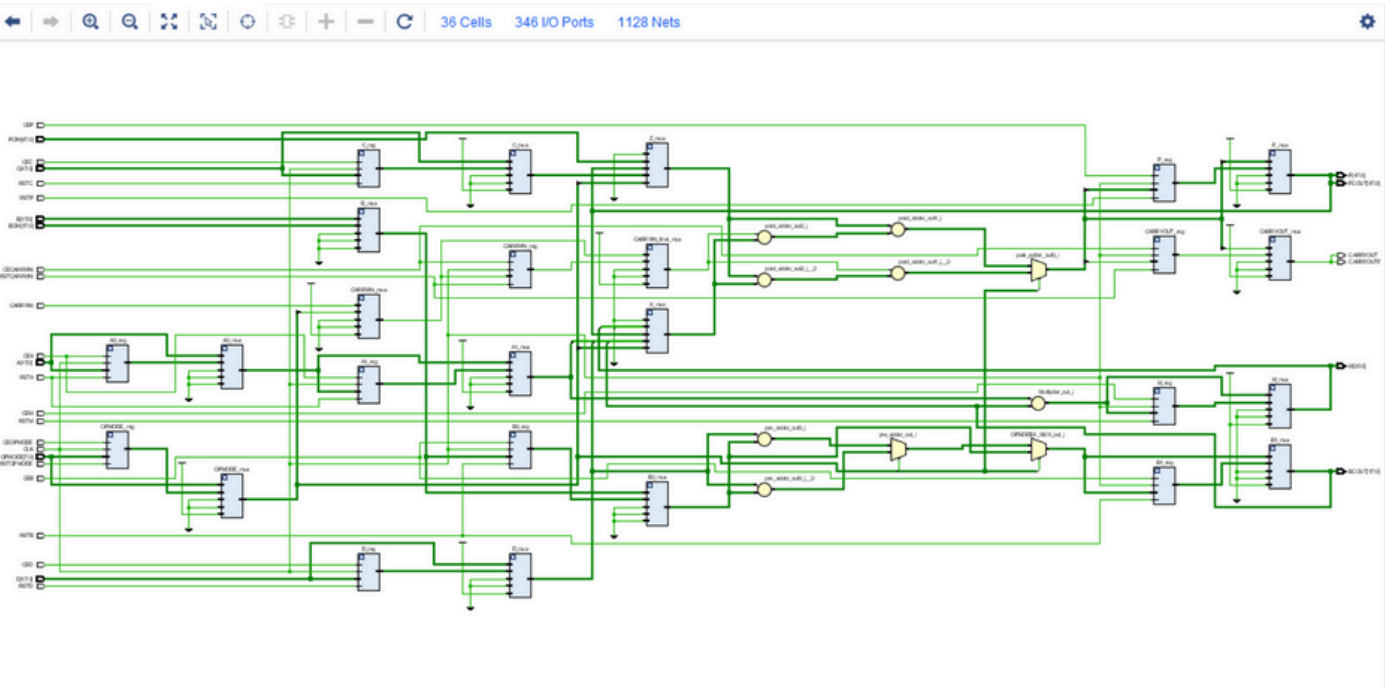

SYNTHESIS

SCHEMATIC

 

TIMING REPORT


General Information	Setup	Hold	Pulse Width
Timer Settings			
Design Timing Summary	Worst Negative Slack (WNS): 5.168 ns	Worst Hold Slack (WHS): 0.182 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Clock Summary (1)	Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
> Check Timing (326)	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
> Intra-Clock Paths	Total Number of Endpoints: 87	Total Number of Endpoints: 87	Total Number of Endpoints: 162
Inter-Clock Paths	All user specified timing constraints are met.		
Other Path Groups			
User Ignored Paths			
> Unconstrained Paths			

UTILIZATION REPORT

Name	Slice LUTs (134600)	Slice Registers (269200)	DSPs (740)	Bonded IOB (500)	BUFGCTRL (32)
DSP48A1	230	160	1	327	1
A1_reg (REG)	0	18	0	0	0
B1_reg (REG_0)	0	18	0	0	0
C_reg (REG_paramet...)	0	48	0	0	0
CARRYIN_reg (REG_...)	1	1	0	0	0
CARRYOUT_reg (REG_...)	0	1	0	0	0
D_reg (REG_2)	0	18	0	0	0
OPMODE_reg (REG_...)	229	8	0	0	0
P_reg (REG_paramet...)	0	48	0	0	0

IMPLEMENTATION

SCHEMATIC

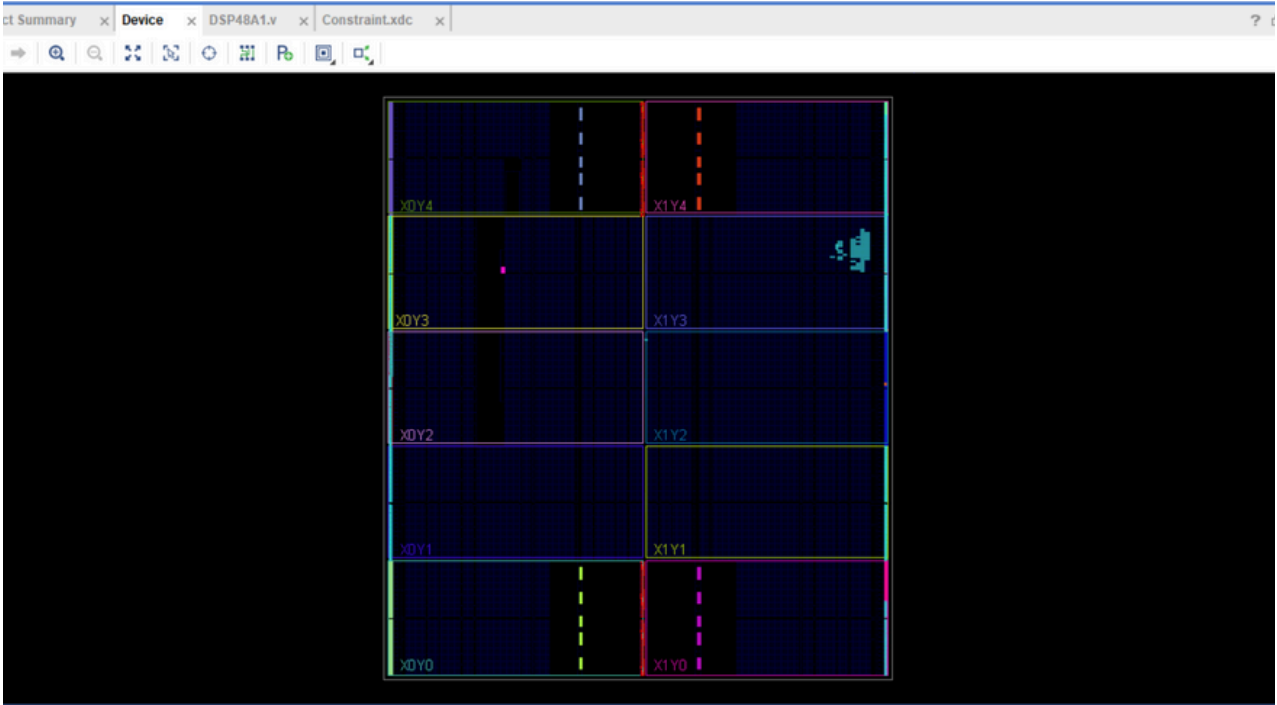

TIMING REPORT

Design Timing Summary			
Setup	Hold	Pulse Width	
Worst Negative Slack (WNS): 3.891 ns	Worst Hold Slack (WHS): 0.273 ns	Worst Pulse Width Slack (WPWS): 4.500 ns	
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns	
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	
Total Number of Endpoints: 106	Total Number of Endpoints: 106	Total Number of Endpoints: 181	
All user specified timing constraints are met.			

UTILIZATION REPORT

Name	Slice LUTs (133800)	Slice Registers (267600)	Slice (33450)	LUT as Logic (133800)	LUT Flip Flop Pairs (133800)	DSP s (740)	Bonded IOB (500)	BUFGCTRL (32)
DSP48A1	230	179	100	230	50	1	327	1
A1_reg (REG)	0	18	6	0	0	0	0	0
B1_reg (REG_0)	0	36	10	0	0	0	0	0
C_reg (REG__paramet...	0	48	16	0	0	0	0	0
CARRYIN_reg (REG____...	1	1	1	1	1	0	0	0
CARRYOUT_reg (REG____...	0	2	2	0	0	0	0	0
D_reg (REG_2)	0	18	10	0	0	0	0	0
OPMODE_reg (REG____...	229	8	74	229	0	0	0	0
P_reg (REG__paramet...	0	48	12	0	0	0	0	0